

Synthesis of an LC two-port terminated in resistance at both ends - Forward divisions - Scaling

1 Synthesis of an LC two-port terminated in resistance at both ends

Consider the following squared module of the transmission coefficient $t(p)$:

$$|t(j\omega)|^2 = \frac{1}{1 + \omega^8} \quad (1)$$

Find the two LC two-ports terminated in resistance at both ends, that realize the given function $|t(j\omega)|^2$.

2 Forward divisions

Using forward divisions, find the circuits corresponding to the following impedances:

a) $Z(s) = \frac{2s^2 + 4s + 3}{s^3 + 2s^2 + 2s + 1}$

b) $Z(s) = \frac{2s^3 + 5s^2 + 36s + 15}{2s^2 + 5s + 30}$

c) $Z(s) = \frac{2s^2 + 3s + 2}{2s^3 + 7s^2 + 9s + 5}$

3 Scaling

Consider the following circuit, where the components values are:

$$C_2 = C_4 = 200 \text{ pF} , \quad L_3 = 3 \mu\text{H} , \quad R_1 = R_4 = 75 \Omega$$

Find the scaling constants R_0 and ω_0 such that the components values became:

$$c_2 = c_4 = 1 \text{ F} , \quad r_1 = r_4 = 1 \Omega.$$

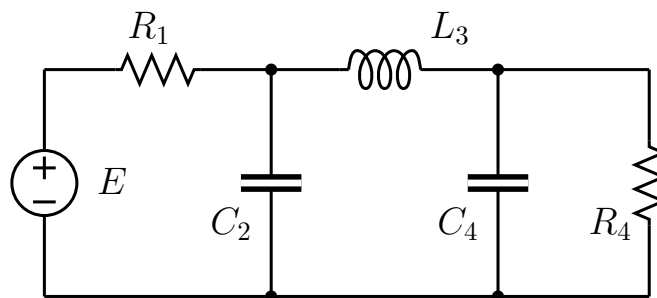


Figure 1: RLC circuit